
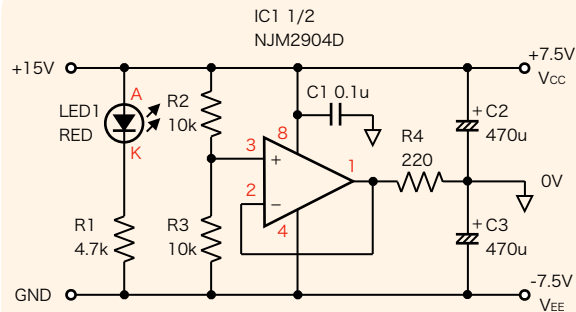


AB級アンプ (その4)

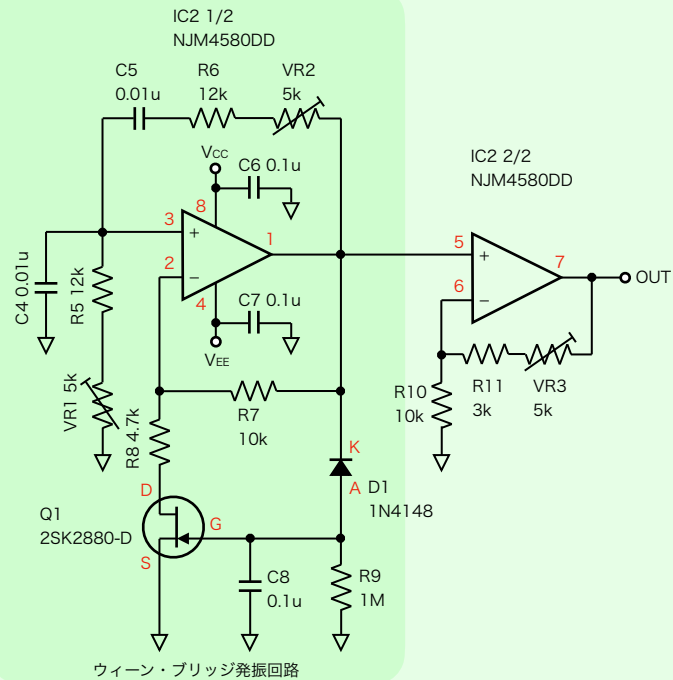


正弦波発生回路用電源回路



ウィーン・ブリッジ発振回路

正弦波発生回路

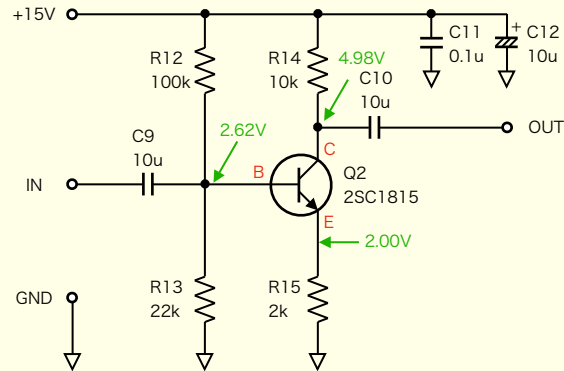

電源電圧 $V_{CC} = 15V$

電圧利得 $A_v = 5$

エミッタ電流 $I_E = 1mA = I_C$

エミッタ電圧 $V_E = 2V$

$V_{BE} = 0.6V$

R_{12} と R_{13} に流す電流 $I = 0.1mA$

$R_E(R_{15}) = V_E/I_E = 2/0.001 = 2,000 = 2k\Omega$

$R_C(R_{14}) = R_E \times A_v = 2,000 \times 5 = 10,000 = 10k\Omega$

$V_C = V_{CC} - I_C \cdot R_C = 15 - 0.001 \times 10,000 = 5V$

$V_{CE} = V_C - V_E = 5 - 2 = 3V$

コレクタ損失 $P_C = V_{CE} \cdot I_C = 3 \times 0.001 = 0.003 = 3mW$

$V_B = V_E + V_{BE} = 2 + 0.6 = 2.6V$

$R_{12} = (V_{CC} - V_B)/I = (15 - 2.6)/0.0001 = 124,000 \approx 100k\Omega$

$R_{13} = V_B/I = 2.6/0.0001 = 26,000 \approx 22k\Omega$

エミッタ接地増幅回路