
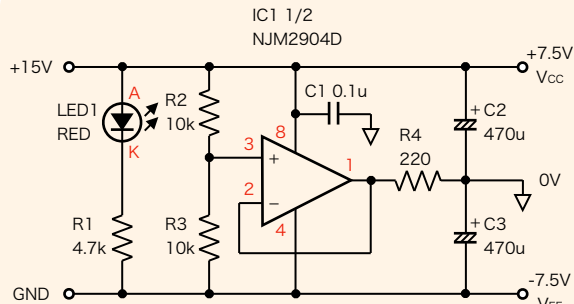



AB級アンプ (その4.2)

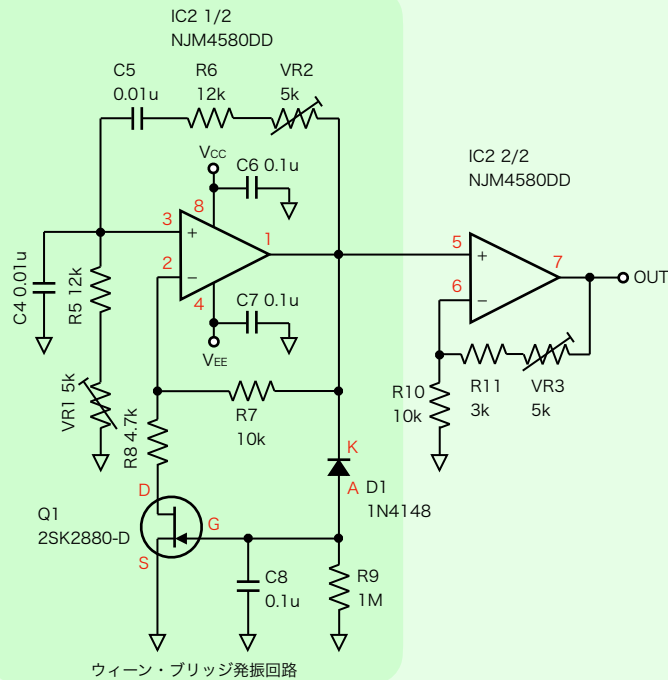

正弦波発生回路用電源回路



正弦波発生回路

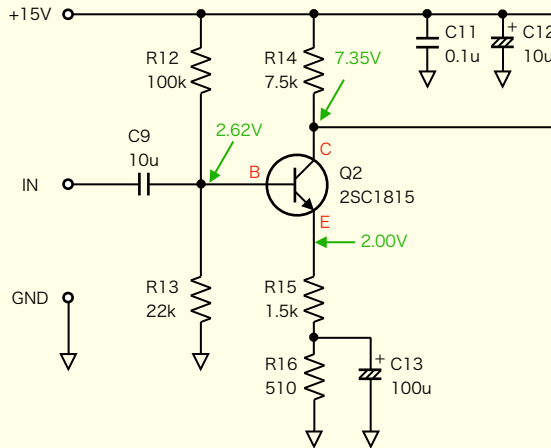

電源電圧 $V_{CC} = 15V$
 電圧利得 $A_v = 5$
 エミッタ電流 $I_E = 1mA = I_C$
 エミッタ電圧 $V_E = 2V$
 コレクタ電圧 $V_C = 7.5V$
 $V_{BE} = 0.6V$
 R_{12} と R_{13} に流す電流 $I = 0.1mA$

$R_C(R_{14}) = (V_{CC} - V_C) / I_C = (15 - 7.5) / 0.001 = 7,500 = 7.5k\Omega$
 $V_C = V_{CC} - I_C \cdot R_C = 15 - 0.001 \times 7,500 = 7.5V$
 $R_E = V_E / I_E = 2 / 0.001 = 2,000 = 2k\Omega$
 $R_{E1}(R_{15}) = R_C / A_v = 7,500 / 5 = 1,500 = 1.5k\Omega$
 $R_{E2}(R_{16}) = R_E - R_{E1} = 2,000 - 1,500 = 500 = 510\Omega$
 $V_{CE} = V_C - V_E = 7.5 - 2 = 5.5V$
 コレクタ損失 $P_C = V_{CE} \cdot I_C = 5.5 \times 0.001 = 0.0055 = 5.5mW$
 $V_B = V_E + V_{BE} = 2 + 0.6 = 2.6V$
 $R_{12} = (V_{CC} - V_B) / I = (15 - 2.6) / 0.0001 = 124,000 \approx 100k\Omega$
 $R_{13} = V_B / I = 2.6 / 0.0001 = 26,000 \approx 22k\Omega$

エミッタ接地増幅回路

最大出力電圧 $5V_{P-P}$
 最大出力電流 $\pm 2.5mA$ ($1k\Omega$ 負荷)
 エミッタ電流 $I_E = 10mA = I_C$
 $h_{FE} = 200$

$V_E = V_B - V_{BE} = 7.35 - 0.6 = 6.75V$
 $V_{CE} = V_{CC} - V_E = 15 - 6.75 = 8.25V$
 コレクタ損失 $P_C = V_{CE} \cdot I_C = 8.25 \times 0.01 = 0.0825 = 82.5mW$
 $R_{E}(R_{17}) = V_E / I_E = 6.75 / 0.01 = 675 = 680\Omega$
 $I_B = I_E / h_{FE} = 0.01 / 200 = 0.00005 = 0.05mA$

エミッタ・フォロウ回路