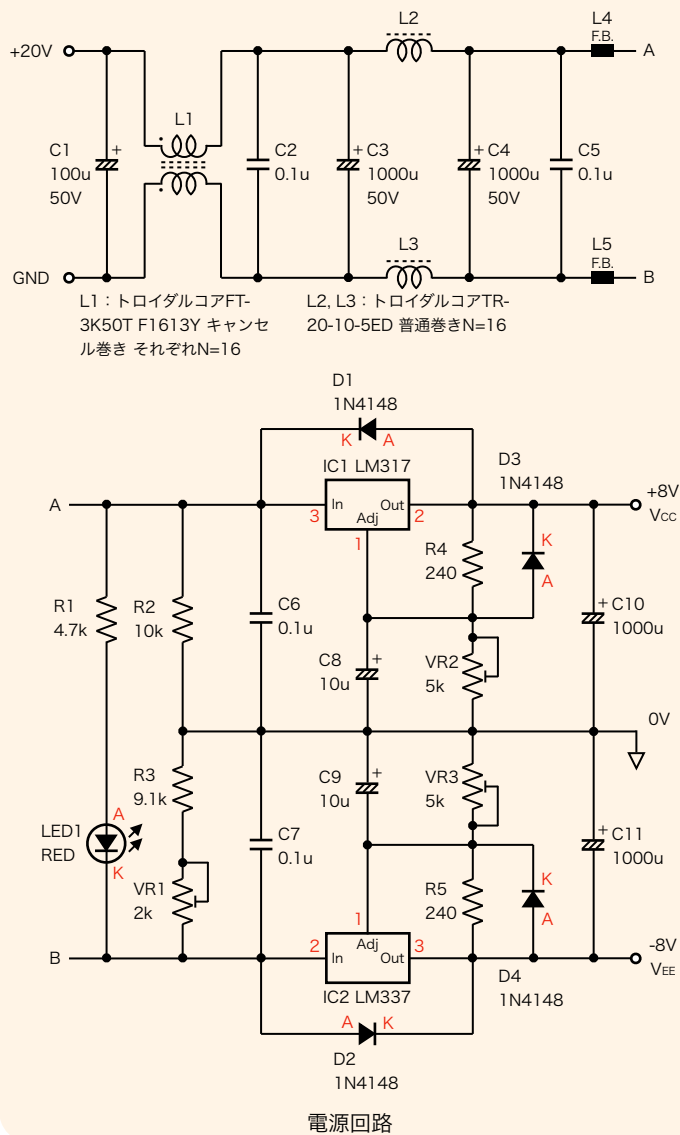


1W+1W AB級アンプ (その6 1/3)



LM317 $V_{Out} = V_{REF}(1 + VR2/R4)$, $VR2 = R4(V_{Out}/V_{REF} - 1)$, $V_{REF} = 1.25V$
 V_{Out} を8Vにする場合 $VR2 = 240(8/1.25 - 1) = 1,296\Omega \dots VR3$ も同じ

